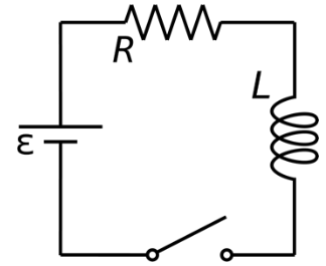



Previously we learned about these [basics of an LR circuit](#):

LR Circuit Limits:

- At $t_{\text{initial}} = 0$; $I_{\text{initial}} = 0$ & $\left(\frac{dI}{dt}\right)_{\text{initial}} = \frac{\epsilon}{L}$ [max value]
- At $t_{\text{final}} \approx \infty$; $I_f = \frac{\epsilon}{R}$ [max value] & $\left(\frac{dI}{dt}\right)_{\text{final}} = 0$



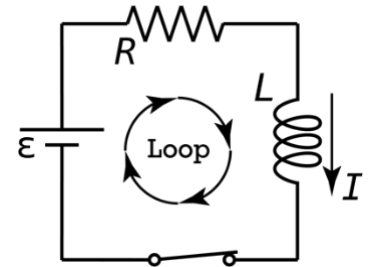Today we are going to derive the equations for current as a function of time and the time rate of change of current as a function of time. To do this we use with Kirchhoff's Loop Rule starting in the lower left-hand corner of the LR circuit.



$$\Delta V_{\text{Loop}} = 0 = \epsilon - \Delta V_R - \Delta V_L = \epsilon - IR - L \frac{dI}{dt}$$

$$\Rightarrow L \frac{dI}{dt} = \epsilon - IR \Rightarrow \frac{L}{R} \frac{dI}{dt} = \frac{\epsilon}{R} - I$$

$$\& \text{ Let } u = \frac{\epsilon}{R} - I \Rightarrow du = -dI \Rightarrow \frac{L}{R} \frac{-du}{dt} = u \Rightarrow \frac{du}{u} = -\frac{R}{L} dt$$

$$\Rightarrow \int \frac{du}{u} = \int -\frac{R}{L} dt \Rightarrow \int_{u_i}^{u_f} \frac{1}{u} du = -\frac{R}{L} \int_0^t dt \Rightarrow \ln u \Big|_{u_i}^{u_f} = -\frac{R}{L} t \Big|_0^t$$

$$\& \int \frac{dx}{x-a} = \ln|x-a| \Rightarrow \int \frac{du}{u} = \ln|u| = \ln u$$

- In this problem $a = 0$ and, because I varies from 0 to $\frac{\epsilon}{R}$, u is always positive (or zero).

$$\Rightarrow \ln u_f - \ln u_i = \ln\left(\frac{u_f}{u_i}\right) = -\frac{R}{L} t \Rightarrow e^{\left(\ln\left(\frac{u_f}{u_i}\right)\right)} = e^{\left(-\frac{R}{L} t\right)} \Rightarrow \frac{u_f}{u_i} = e^{\left(-\frac{Rt}{L}\right)}$$

$$\Rightarrow u_f = u_i e^{\left(-\frac{Rt}{L}\right)} \& u_f = \frac{\epsilon}{R} - I_f \& u_i = \frac{\epsilon}{R} - I_i = \frac{\epsilon}{R}$$

$$\Rightarrow \frac{\epsilon}{R} - I_f = \frac{\epsilon}{R} e^{\left(-\frac{Rt}{L}\right)} \Rightarrow -I_f = -\frac{\epsilon}{R} + \frac{\epsilon}{R} e^{\left(-\frac{Rt}{L}\right)} \Rightarrow I_f = \frac{\epsilon}{R} - \frac{\epsilon}{R} e^{\left(-\frac{Rt}{L}\right)}$$

$$\Rightarrow I(t) = \frac{\epsilon}{R} \left(1 - e^{\left(-\frac{Rt}{L}\right)}\right) = I_{\text{max}} \left(1 - e^{\left(-\frac{Rt}{L}\right)}\right)$$

Note, this fits our limits because:

- $I(0) = \frac{\epsilon}{R} \left(1 - e^{\left(-\frac{R(0)}{L}\right)}\right) = \frac{\epsilon}{R} (1 - e^0) = \frac{\epsilon}{R} (1 - 1) = 0$

- $I(\infty) = \frac{\epsilon}{R} \left(1 - e^{\left(-\frac{R(\infty)}{L}\right)}\right) = \frac{\epsilon}{R} (1 - e^{-\infty}) = \frac{\epsilon}{R} (1 - 0) = \frac{\epsilon}{R}$

We can also determine the time rate of change of current as a function of time:

$$I_f = \frac{\epsilon}{R} - \frac{\epsilon}{R} e^{\left(-\frac{Rt}{L}\right)} \Rightarrow \frac{dI}{dt} = \frac{d}{dt} \left(\frac{\epsilon}{R} - \frac{\epsilon}{R} e^{\left(-\frac{Rt}{L}\right)} \right) = \left(-\frac{\epsilon}{R} \right) \frac{d}{dt} e^{\left(-\frac{Rt}{L}\right)} = - \left(\frac{\epsilon}{R} \right) \left(\frac{R}{L} \right) e^{\left(-\frac{Rt}{L}\right)}$$
$$\Rightarrow \frac{dI}{dt} (t) = \frac{\epsilon}{L} e^{\left(-\frac{Rt}{L}\right)} = \left(\frac{dI}{dt} \right)_{\max} e^{\left(-\frac{Rt}{L}\right)} \quad \& \quad \frac{d}{dx} (e^{ax}) = a e^{ax}$$

Again, this fits our limits because:

$$\frac{dI}{dt} (0) = \frac{\epsilon}{L} e^{\left(-\frac{R(0)}{L}\right)} = \frac{\epsilon}{L} e^0 = \frac{\epsilon}{L} \quad \& \quad \frac{dI}{dt} (\infty) = \frac{\epsilon}{L} e^{\left(-\frac{R(\infty)}{L}\right)} = \frac{\epsilon}{L} e^{-\infty} = 0$$