

AP Physics C: E + M Notes

$$F_e = \frac{kq_1 q_2}{r^2}$$

$$E = \frac{F_e}{q} = \frac{kq}{r^2} \text{ (Point Charge)}$$

- start @ +q & end @ -q
- never loops (or ∞)

- \perp to surface

$$\rho = \frac{Q}{V}; \sigma = \frac{Q}{A}; \lambda = \frac{Q}{L}$$

$$\Phi_E = \int E \cdot dA = EA \cos \theta \text{ (constant } A, E, \theta)$$

$$\Phi_E = \oint E \cdot dA = \frac{q_{\text{in}}}{\epsilon_0}$$

Gaussian Surface!

emf vs. ΔV_E

$$(\text{Ideal } \Delta V \text{ only w/ } I=0) \quad (\Delta V_E = E - Ir)$$


$$R_{\parallel} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$

(ΔV same, I add)

$$R_{\text{series}} = R_1 + R_2 + \dots$$

(I same & ΔV add)

Kirchhoff's Rules

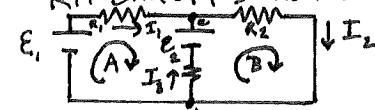

$$\text{@ Junction Loop } \sum I_{\text{in}} = \sum I_{\text{out}}$$

$$\Delta V_{\text{loop}} = 0$$

$$\tau = NIA \times \vec{B}$$

$$= NIAB \sin \theta$$

$$\Rightarrow F_B = IL' \times \vec{B}$$

(in constant B field
 L' \Rightarrow straight line)

$$F_B = I \oint d\vec{s} \times \vec{B} = I(0) \times B$$

$$= 0 \text{ (Loop in Constant } B \text{ field)}$$

V_{\perp} to B field

Circular Motion

$$\sum F_{\text{in}} = ma_r \& \omega = \frac{2\pi}{T}$$

$$dB = \frac{\mu_0}{4\pi} \frac{I dI \times \vec{r}}{r^2}$$

B field @ center of an Arc.
& @ Axis of a Loop.

$$E_L = -L \frac{dI}{dt}$$

$$\Delta V = IR$$

RL Circuit

$$I(t) = \frac{E}{R}(1 - e^{-\frac{Rt}{L}})$$

$$\frac{dI}{dt}(t) = \frac{E}{L}(e^{-\frac{Rt}{L}})$$

Putting energy into L

$$I(0) = 0 \& \frac{dI}{dt}(0) = \frac{E}{L}$$

$$I(\infty) = \frac{E}{R} \& \frac{dI}{dt}(\infty) = 0$$

$$U_{\text{ele}} = \frac{kq_1 q_2}{r}$$

$$\Delta V = \frac{\Delta U_{\text{ele}}}{q} = \frac{kq}{r} \text{ (Point Charge)}$$

$$dV = \frac{kq}{r} \text{ (continuous Charge Distribution)}$$

Scalar!

$$\Delta V = - \int E \cdot dr = - \frac{E \Delta d}{(\text{const E field})}$$

$$1 \text{ electron Volt} = 1.6 \times 10^{-19} \text{ J}$$

$$C \equiv \frac{Q}{\Delta V} = \frac{\kappa \epsilon_0 A}{d}$$

(II Plate w/
dielectric)

$$\Delta V_A = E_1 - \Delta V_{R_1} - E_2 + \Delta V_{R_3} = 0$$

$$= E_1 - I_1 R_1 - E_2 + I_3 R_3 = 0$$

$$\Delta V_B = 0 = E_2 - \Delta V_{R_2} - \Delta V_{R_3}$$

$$0 = E_2 - I_2 R_2 - I_3 R_3$$

$$\sum I_{\text{in}} = \sum I_{\text{out}} \text{ Junction law}$$

$$I_1 + I_3 = I_2$$

RC Circuit

$$q(t) = Q_i (e^{-t/RC})$$

$$I(t) = \frac{E}{R} e^{-t/RC}$$

charging

$$t \approx 0 \Rightarrow I = I_{\text{max}} \& Q = 0$$

$$t \approx \infty \Rightarrow I \approx 0 \& Q \approx Q_{\text{max}}$$

$$B_s = \frac{\mu_0 NI}{L} \text{ (solenoid)}$$

$$\oint B \cdot d\vec{s} = \mu_0 I_{\text{in}}$$

$$B = \frac{\mu_0 I}{2\pi r}$$

2 || Current Carrying Wires

$$F_B = I_1 l \times B_2 = I_1 l B_2 \sin 90^\circ$$

$$= I_1 l \frac{\mu_0 I_2}{2\pi r}$$

$$F_B = \frac{I_1 I_2 \mu_0 l}{2\pi r}$$

$$\oint B \cdot dA = 0$$

$$\oint B \cdot dA = BA \cos \theta$$

Removing Energy from L

$$I(t) = \frac{E}{R} e^{-\frac{Rt}{L}}$$

$$\frac{dI}{dt}(t) = -\frac{E}{L} e^{-\frac{Rt}{L}}$$

$$I(0) = \frac{E}{R} \frac{dI}{dt}(0) = \frac{E}{L}$$

$$I(\infty) = 0 \frac{dI}{dt}(\infty) = 0$$

$$U_L = \frac{1}{2} L I^2$$

LC Circuit

$$\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q$$

$$\omega = \sqrt{\frac{1}{LC}} = \frac{2\pi}{T}$$

$$C_{\text{series}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots \right)^{-1}$$

(Q same & ΔV add)

$$C_{\parallel} = C_1 + C_2 + \dots$$

(ΔV same & Q add)

$$U_c = \frac{Q^2}{2C} = \frac{1}{2} C \Delta V^2 = \frac{1}{2} Q \Delta V$$

$$I = \frac{dQ}{dt} = N q V \perp A$$

$$\Delta V = IR \Rightarrow R = \frac{\Delta V}{I}$$

$$R = \frac{\rho l}{A}$$

$$P = I \Delta V = I^2 R = \frac{\Delta V^2}{R}$$

Ammeter in series

(Low R: Same I)

Voltmeter: in ||

(High R: Same ΔV)

$$F_B = q \vec{v} \times \vec{B} \not\parallel RHR$$

$$= q v B \sin \theta$$

$$= IL \times \vec{B} = ILB \sin \theta$$

discharging

$$q(t) = Q_i (e^{-t/RC})$$

$$I(t) = -I_i e^{-t/RC}$$

$$t \approx 0 \Rightarrow I = I_{\text{max}} \& Q = Q_{\text{max}}$$

$$t \approx \infty \Rightarrow I \approx 0 \& Q \approx 0$$

$$\tau = RC \text{ (63.2%)} \text{ (63.2%)}$$

$$(1 - e^{-t/RC}) = (1 - e^{-1}) = 0.632$$

$$E = -N \frac{d\Phi_B}{dt} = -N \frac{d}{dt} (BA \cos \theta)$$

Lenz' Law



B induced out
I_{ind} is CCW

Motional Emf $\Delta V = VB \sin \theta$

θ b/wn \vec{v} & \vec{B}

$$E_{\text{gen}} = \omega N B A \sin \omega t = E_{\text{back emf}}$$

$$E_L = -L \frac{dI}{dt} = -N \frac{d\Phi_B}{dt} \Rightarrow L = \frac{N \Phi_B}{I}$$

$$Q(t) = Q_{\text{max}} \cos(\omega t + \phi)$$

$$I = \frac{dQ}{dt}$$

SHM \Rightarrow Conservation of Energy.

