

# The Law of Charges

1

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

$$I \equiv \frac{dq}{dt} \left( \frac{C}{s} \right) \text{ Ampere, A} \quad \Delta V = 0 \rightarrow \text{no current flow}$$

$$I \equiv \frac{\Delta Q}{\Delta t} \quad \text{Base SI}$$

Conventional current

+ is w/ the dir that + charges would flow  
 $e^-$  flow, + opp of +

P.833 |  $I = \frac{\Delta Q}{\Delta t}$   $\Delta Q = \# \text{ of charge carriers} \times \text{charge/carrier}$

$$I = \frac{N A V_d \Delta t q}{\Delta t}$$

$N = \# \text{ of charge carriers/volume}$

charge carrier density

$$\Delta Q = N V q = N A \Delta x q$$

$$\Delta Q = N A V_d \Delta t q$$

$$I = N A V_d q$$

$$V = A \Delta x$$

$$V = \frac{\Delta x}{\Delta t}$$

$$\Delta x = V_d \Delta t$$

$$V_d = \text{drift velocity} \approx 0.1 \text{ mm/s}$$

Derivation of Resistance and Resistivity (with Example)

2

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

$J = \frac{I}{A} = \frac{N A V_d q}{A} \rightarrow J = N V_d q$   
 Current Density

$J = \sigma E$   
 Ohmic, or follow Ohm's law  
 $\sigma = \text{conductivity}$   
 $\rho = \frac{1}{\sigma}$  resistivity

$||\Delta V|| = E d$   
 $\Delta V = E l$   
 $E = \frac{\Delta V}{l}$   
 $\rightarrow J = \sigma \frac{\Delta V}{l}$   
 $\Delta V = \frac{J l}{\sigma}$   
 $\Delta V = \frac{I l}{A \sigma}$   
 $\Delta V = \left(\frac{l}{A \sigma}\right) I$   
 resistance

$\Delta V = \frac{\rho l}{A} I$   
 resistance  
 $R = \frac{\rho l}{A}$   
 $\Delta V = I R$   
 $R = \frac{\Delta V}{I} \left(\frac{V}{A}\right)$   
 $\frac{V}{A} = \Omega \text{ ohms}$

Resistance  $\Delta V = I R + R = \frac{\rho l}{A} \rightarrow \text{object-specific}$

Resistivity  $\rho \rightarrow \text{material property}$

$$\rho = \frac{R A}{l} \rightarrow \frac{\Omega m^2}{m} = \Omega m$$

Ex)  $\Delta V = 12 \text{ V}$       $R = \frac{\rho l}{A}$       $\rho = 2.82 \times 10^{-8} \Omega m$   
 $l = 25 \text{ m}$       $R = \frac{(2.82 \times 10^{-8})(25)}{\pi (0.001)^2}$       $A = \pi r^2$   
 $d = 0.001 \text{ m}$   
 Aluminum  
 $R = ?$       $I = ?$       $R = 0.898 \Omega$

$$\Delta V = I R$$

$$I = \frac{\Delta V}{R} = \frac{12}{0.898} = 13.4 \text{ A}$$

Derivation of Electric Power and KiloWatt Hours (with Example)

3

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

$$P = \frac{dU}{dt} = \frac{d}{dt}(q \Delta V)$$

$$P = \frac{dq}{dt} \Delta V$$

$$P = I \Delta V$$

$$= I(IR) = I^2 R$$

$$P = I \Delta V = I^2 R = \frac{\Delta V^2}{R}$$

$$= \left(\frac{\Delta V}{R}\right) R = \frac{\Delta V^2}{R}$$

Ex]  $\Delta V = 120 \text{ V}$  (standard)

100 watt + 60 watt

$R_{100} = ?$   $R_{60} = ?$

$$R_{100} = \frac{120^2}{100} = 144 \Omega$$

$$P = \frac{\Delta V^2}{R}$$

$$R = \frac{\Delta V^2}{P}$$

$$R_{60} = \frac{120^2}{60} = 240 \Omega$$

my monitor

$I = 1.5 \text{ A}$

10¢/kwhr

8 hrs/day

$\Delta V = 120 \text{ V}$

$$P = I \Delta V = 1.5(120) = 180 \text{ W} = 0.180 \text{ kW}$$

$$0.180 \text{ kW}(8 \text{ hr}) = 1.44 \text{ kwhr}$$

$$1.44 \text{ kwhr} \left( \frac{10 \text{ ¢}}{\text{kwhr}} \right) = 14.4 \text{ ¢}$$

$$\text{kwhr} \left( \frac{1000 \text{ W}}{1 \text{ kW}} \right) = 1000 \text{ W/hr} = 1000 \frac{\text{J}}{\text{s}} \text{ hr}$$

$$1000 \frac{\text{J}}{\text{s}} \text{ hr} \left( \frac{3600 \text{ s}}{1 \text{ hr}} \right) = \boxed{3.6 \times 10^6 \text{ J}} \quad \text{kwhr is energy}$$

Problem 27-4 Bohr Model of Hydrogen Atom - Velocity of Electron and Effective Current

4

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

$$27-4) r = 5.29 \times 10^{-11} \text{ m}$$

$$\Sigma F_{in} = F_e = m a_c$$

$$\frac{k_e q_e q_p}{r^2} = m \frac{v^2}{r}$$

$$\frac{k_e q^2}{r} = m v^2$$

$$v = \sqrt{\frac{k_e q^2}{r m}} = \sqrt{\frac{(8.99 \times 10^9)(1.60 \times 10^{-19})^2}{(5.29 \times 10^{-11})(9.11 \times 10^{-31})}} = 2.19 \times 10^6 \text{ m/s}$$

$$v = r \omega \quad I = \frac{\Delta Q}{\Delta t} = \frac{q}{2\pi / \omega} = \frac{q}{2\pi / r} = \frac{qv}{2\pi r} = \frac{(1.6 \times 10^{-19})(2.19 \times 10^6)}{2\pi(5.29 \times 10^{-11})}$$

$$\omega = \frac{v}{r}$$

$$\omega = \frac{2\pi}{T}$$

$$T = \frac{2\pi}{\omega}$$

$$I = 0.001054 \text{ A}$$

$$I = 1.05 \text{ mA}$$

Introduction to Electromotive Force and Terminal Voltage

5

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

Electromotive force, emf,  $\mathcal{E}$

Ideal, max voltage

$\Delta V_t \rightarrow$  terminal voltage

(voltage across the terminal voltage)

All real batteries have an internal resistance,  $r$

p.860 |  $\Delta V_t = \mathcal{E} - \Delta V_r$

$$\Delta V_t = \mathcal{E} - Ir$$

As  $I \uparrow$ ,  $\Delta V_t \downarrow$

$$\Delta V_t = \mathcal{E} \quad \text{if } I=0$$

Derivation of Resistors in Series and Parallel (with Example)


6

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

2 resistors in series

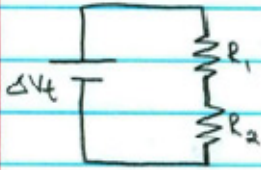

$$I_1 = I_2 = I_t \quad \Delta V = IR$$

$$\Delta V_t = \Delta V_1 + \Delta V_2$$

$$I_t R_{eq} = I_1 R_1 + I_2 R_2$$

$$R_s = R_1 + R_2 + \dots$$

2 resistors in parallel




$$I_t = I_1 + I_2 \quad I = \frac{\Delta V}{R}$$

$$\Delta V_t = \Delta V_1 = \Delta V_2$$

$$\frac{\Delta V_t}{R_{eq}} = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$

$$R_{||} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$

Ex 1

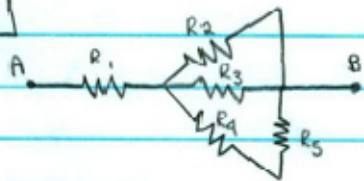

$$R_{45} = R_4 + R_5 = 4 + 5 = 9 \Omega$$

$$R_{2345} = \left( \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_{45}} \right)^{-1} = \left( \frac{1}{2} + \frac{1}{3} + \frac{1}{9} \right)^{-1} = 1.0588$$

$$\Delta V_{ab} = 25V$$

$$R_{eq} = ?$$

$$I_3 = ?$$

$$R_{eq} = R_1 + R_{2345} = 1 + 1.0588 = 2.0588 \Omega$$

$$\Delta V = IR$$

$$25 = I_{eq}(2.0588)$$

$$I_{eq} = 12.143 A = I_1 = I_{2345}$$

$$\Delta V = IR$$

$$\Delta V = 12.143(1.0588)$$


$$\Delta V = 12.857 = \Delta V_2 = \Delta V_3 = \Delta V_5$$

$$\Delta V = IR$$

$$12.857 = I(9)$$

$$I_3 = 1.429 A$$

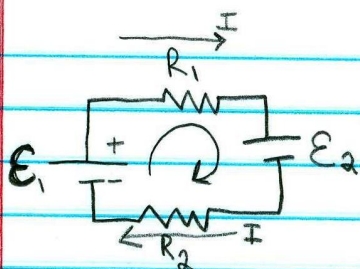Introduction to Kirchoff's Rules (with Example) - 7  
 AP Physics C – Video Lecture Notes - Chapter 27-28  
 Thank You, Emily Rencsok, for these notes.



Kirchoff's Rules

1)  $\Delta V_{loop} = 0$

2)  $\sum I_{in} = \sum I_{out}$  of a junction

$E_1 = 12V$

$E_2 = 8V$

$R_1 = 4 \Omega$

$R_2 = 6 \Omega$

Charging 2nd battery


$\Delta V_{loop} = 0 = +E_1 - \Delta V_{R1} - E_2 - \Delta V_{R2}$

$0 = E_1 - IR_1 - E_2 - IR_2$

$0 = 12 - I(4) - 8 - I(6)$

$0 = 4 - 10I$

$I = 4/10 = \boxed{0.40 A}$

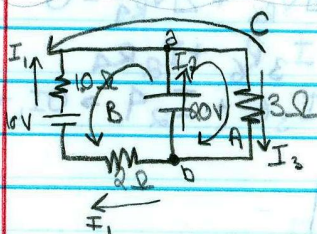

Junction a:  $\sum I_{in} = \sum I_{out}$

$I_1 + I_2 = I_3$

Junction b:  $\sum I_{in} = \sum I_{out}$

$I_3 = I_1 + I_2$

$\Delta V_A = \sum \epsilon - \Delta V_{res} = 0$

$0 = \epsilon_{20} - I_3 R_3$

$0 = 20 - I_3(3)$

$I_3 = \frac{20}{3} A$

$\Delta V_B = 0 = \epsilon_{20} + \Delta V_{R1} - \epsilon_{10} + \Delta V_{R2}$

$0 = \epsilon_{20} + I_1 R_1 - \epsilon_{10} + I_1 R_2$

$0 = 20 + I_1(1) - 10 + I_1(2)$

$0 = 10 + 3I_1$

$I_1 = -10/3 A$

$I_1 + I_2 = I_3$

$-\frac{10}{3} + I_2 = \frac{20}{3}$

$I_2 = \frac{30}{3} = 10 A$

$I_1 = \frac{10}{3} A$  down through  $R_1$

$I_2 = 10 A$  up through  $E_{20}$

$I_3 = \frac{20}{3} A$  down through  $R_3$


$$\Delta V_C = 0 = -\mathcal{E}_{10} + \Delta V_{R_2} + \Delta V_{R_3} + \Delta V_{R_1}$$

$$0 = -\mathcal{E}_{10} + I_1 R_2 + I_3 R_3 + I_1 R_1$$

$$0 = -10 + \frac{10}{3}(2) + \frac{20}{3}(3) + \frac{10}{3}(1)$$


$$0 = -10 - \frac{20}{3} + 20 - \frac{10}{3}$$

$$0 = 0$$

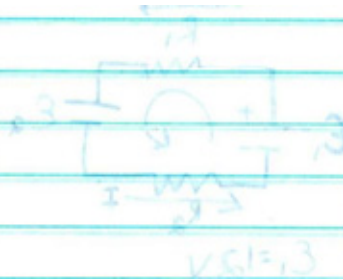



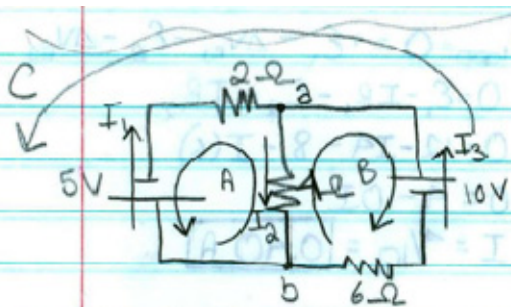A Kirchhoff's Rules Example Problem  
 8  
 AP Physics C – Video Lecture Notes  
 Chapter 27-28  
 Thank You, Emily Rencsok, for these notes.



$$\Delta V_A = +E_5 + \Delta V_{R_2} + \Delta V_{R_4} = 0$$

$$0 = +E_5 + I_1 R_2 + I_2 R_4$$

$$0 = I_2 4 + I_1 2 + 5 \rightarrow 2I_1 + 4I_2 + 0I_3 = -5$$

$$\Delta V_B = -E_{10} + \Delta V_{R_6} + \Delta V_{R_4} = 0$$

$$0 = -E_{10} + I_3 R_6 + I_2 R_4$$

$$0 = -10 + I_3 6 + I_2 4 \rightarrow 0I_1 + 4I_2 + 6I_3 = 10$$

Junction a  $\Sigma I_{in} = \Sigma I_{out}$

$$I_1 + I_3 = I_2$$

$$I_1 - I_2 + I_3 = 0$$

$$\begin{bmatrix} 1 & -1 & 1 & 0 \\ 2 & 4 & 0 & -5 \\ 0 & 4 & 6 & 10 \end{bmatrix}$$

↓ rref

$$\begin{bmatrix} 1 & 0 & 0 & -2.045 \\ 0 & 1 & 0 & -0.227 \\ 0 & 0 & 1 & 1.81 \end{bmatrix}$$

$$\Delta V_C = E_{10} + \Delta V_{R_2} + E_5 - \Delta V_{R_6} = 0$$

$$0 = E_{10} + I_1 R_2 + E_5 - I_3 R_6$$

$$0 = 10 + (-2.045)(2) + 5 - (1.81)(6)$$

$$0 = 0$$

$I_1 = 2.05$  A down through  $E_5$

$I_2 = 0.227$  A up through  $R_4$

$I_3 = 1.81$  A up through  $E_{10}$

RC Circuit - Charging a Capacitor through a Resistor


9

AP Physics C - Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

RC Circuit | Charging a capacitor through a resistor

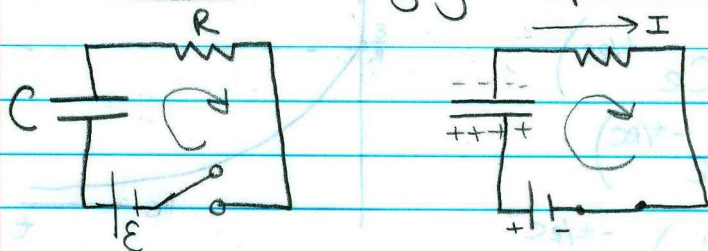

$$C = \frac{Q}{\Delta V} \quad q_i = 0$$

$$\Delta V = \frac{Q}{C} \quad \epsilon = 0$$

$$\Delta V_{\text{loop}} = 0 = +\epsilon - \Delta V_C - \Delta V_R$$

$$0 = \epsilon - \frac{q}{C} - IR$$

$$IR = \epsilon - \frac{q}{C}$$

$$I = \frac{\epsilon}{R} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{\epsilon C}{RC} - \frac{q}{RC}$$

$$\frac{dq}{dt} = \frac{1}{RC} (\epsilon C - q)$$

$$\frac{dq}{dt} = -\frac{1}{RC} (q - \epsilon C)$$

$$\int_0^q \frac{1}{q - \epsilon C} dq = \int_0^t \frac{1}{RC} dt$$

$$\ln(q - \epsilon C) \Big|_0^q = -\frac{1}{RC} \int_0^t dt$$

$$\ln(q - \epsilon C) - \ln(0 - \epsilon C) = -\frac{t}{RC}$$

$$\ln\left(\frac{q - \epsilon C}{-\epsilon C}\right) = -\frac{t}{RC}$$

$$\frac{q - \epsilon C}{-\epsilon C} = e^{-\frac{t}{RC}}$$

$$q - \epsilon C = e^{-\frac{t}{RC}} (-\epsilon C)$$

$$q = -\epsilon C e^{-\frac{t}{RC}} + \epsilon C$$

$$q(t) = \epsilon C (1 - e^{-t/RC})$$

$$0 = \epsilon - IR$$

$$IR = \epsilon$$

$$I_i = \frac{\epsilon}{R} = I_{\text{max}}$$


$$@ t \approx \infty \quad I_f = 0$$

$$q_f = Q$$

$$0 = \epsilon - \frac{q}{C} = 0$$

$$\frac{q}{C} = \epsilon$$

$$Q = \epsilon C = Q_{\text{max}}$$

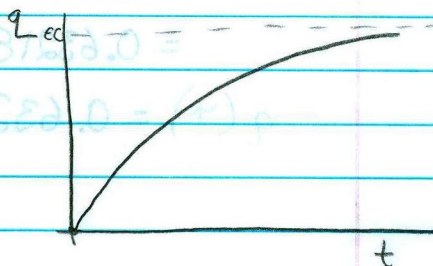


$$I(t) = ? = \frac{dq}{dt}$$

$$I = \frac{d}{dt}(\epsilon C - \epsilon C e^{-t/RC})$$

$$I = \frac{d}{dt}(-\epsilon C e^{-t/RC})$$

$$I = -\epsilon C \left(-\frac{1}{RC}\right) e^{-t/RC}$$

$$I(t) = \frac{\epsilon}{R} e^{-t/RC}$$

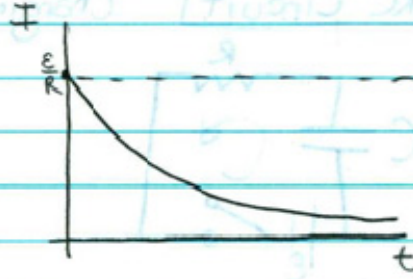

RC Circuit - Definition of the Time Constant

10

AP Physics C - Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

Time constant,  $\tau$

$$\tau = RC \rightarrow \Omega F$$

$$= \frac{V}{A} \left( \frac{C}{V} \right)$$

$$= \frac{C}{A}$$

$$= \frac{C}{e/s} = \text{seconds}$$

$$q(t) = EC(1 - e^{-t/RC})$$

$$q(\tau) = EC(1 - e^{-RC/RC})$$

$$= EC(1 - e^{-1})$$

$$= EC(1 - 0.3678)$$

$$= 0.6321EC$$

$$q(\tau) = 0.632 Q_{\max}$$

KNOW THIS #!!



Time for a 63.2% change


Another Kirchhoff's Rules Example Problem

11

AP Physics C – Video Lecture Notes

Chapter 27-28

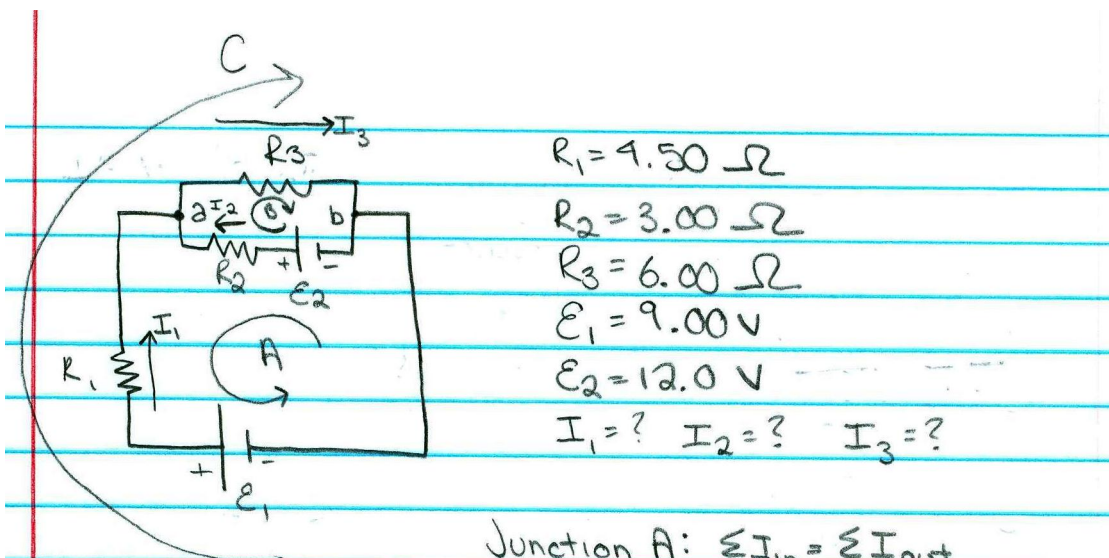Thank You, Emily Rencsok, for these notes.



$$R_1 = 4.50 \, \Omega$$

$$R_2 = 3.00 \, \Omega$$

$$R_3 = 6.00 \, \Omega$$

$$\mathcal{E}_1 = 9.00 \, \text{V}$$

$$\mathcal{E}_2 = 12.0 \, \text{V}$$

$$I_1 = ? \quad I_2 = ? \quad I_3 = ?$$

Junction A:  $\sum I_{in} = \sum I_{out}$

$$I_1 + I_2 = I_3$$

$$I_1 + I_2 - I_3 = 0$$

$$4.5I_1 + 3I_2 - 0I_3 = -3$$

$$0I_1 - 3I_2 - 6I_3 = -12$$

$$\Delta V_A = 0 = +\Delta V_{R1} - \mathcal{E}_1 + \mathcal{E}_2 - \Delta V_{R2}$$

$$0 = I_1 R_1 - \mathcal{E}_1 + \mathcal{E}_2 - I_2 R_2$$

$$0 = I_1(4.5) - 9 + 12 - I_2(3)$$

$$\Delta V_B = 0 = -\Delta V_{R3} + \mathcal{E}_2 - \Delta V_{R2}$$

$$0 = \mathcal{E}_2 - I_2 R_2 - I_3 R_3$$

$$0 = 12 - I_2(3) - I_3(6)$$


$$\begin{bmatrix} 1 & 1 & -1 & 0 \\ 4.5 & -3 & 0 & -3 \\ 0 & -3 & -6 & -12 \end{bmatrix} \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0.153846 \\ 0 & 1 & 0 & 1.23076 \\ 0 & 0 & 1 & 1.38461 \end{bmatrix}$$

$$\begin{aligned} I_1 &= 1.54 \, \text{mA} && \text{up through } R_1 \\ I_2 &= 1.23 \, \text{A} && \text{left through } R_2 \\ I_3 &= 1.38 \, \text{A} && \text{right through } R_3 \end{aligned}$$

Row Reduced Echelon Form

RC Circuit - Discharging a Capacitor through a Resistor - 12  
 AP Physics C - Video Lecture Notes  
 Chapter 27-28  
 Thank You, Emily Rencsok, for these notes.

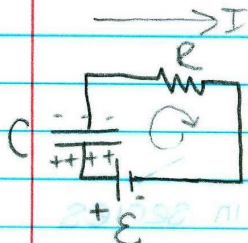Discharging a capacitor through a resistor



$$\Delta V_{loop} = 0 = \mathcal{E} - \Delta V_C - \Delta V_R$$

$$0 = \mathcal{E} - \frac{q}{C} - IR$$

$q(t) = ?$   
 $I(t) = ?$

Removed battery

$C = \frac{q}{\Delta V}$   
 $\Delta V = \frac{q}{C}$

$$0 = -\frac{q}{C} - IR$$

@  $t=0$  close switch

$$IR = -\frac{q}{C}$$

$q_i = Q_{max}$

$$I = -\frac{q}{RC}$$

$I_i = I_{max}$


$$\frac{dq}{dt} = -\frac{q}{RC}$$

@  $t \approx \infty$

$$\int \frac{dq}{q} = \int -\frac{1}{RC} dt$$

$q_f = 0$


$I_f = 0$

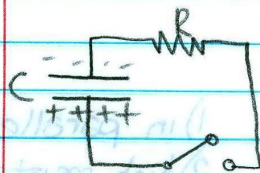

$t=0$   
 close switch

$$[\ln q]_Q^0 = -\frac{1}{RC} \int_0^t dt$$

$$\ln q - \ln Q = -\frac{t}{RC}$$

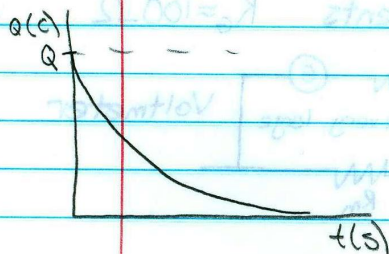

$$\ln \frac{q}{Q} = -\frac{t}{RC}$$

$$\frac{q}{Q} = e^{-t/RC}$$

$$q(t) = Q e^{-t/RC}$$

$$I = \frac{dq}{dt} = \frac{d}{dt} (Q e^{-t/RC})$$

$$I(t) = -\frac{Q}{RC} e^{-t/RC}$$


$Q_i = \mathcal{E}C$

$$I(t) = -\frac{\mathcal{E}C}{RC} e^{-t/RC}$$

$$I(t) = -\frac{\mathcal{E}}{R} e^{-t/RC}$$

$$I(t) = -I_i e^{-t/RC}$$

↑  
 discharging

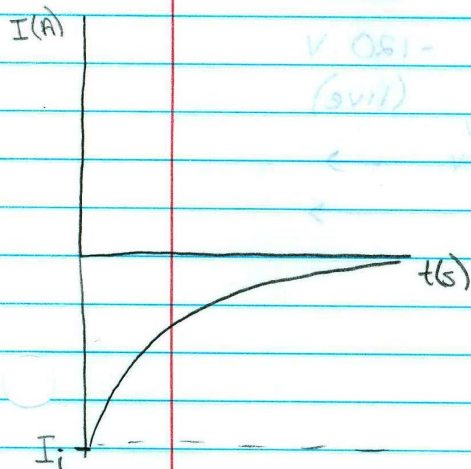

Ammeters, Voltmeters, Galvanometers and Household Circuits

13



AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.


\* Ammeter + voltmeter

Ammeter

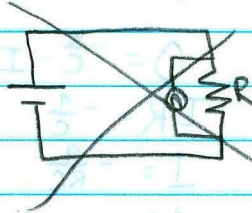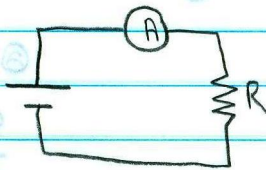



- 1) in series
- 2) small resistance

Voltmeter

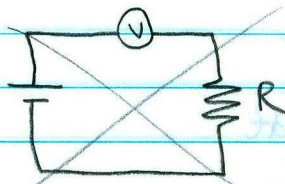

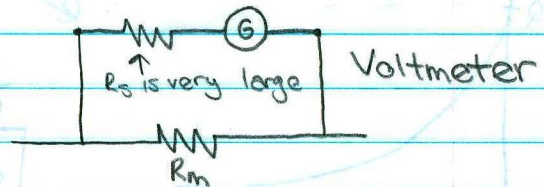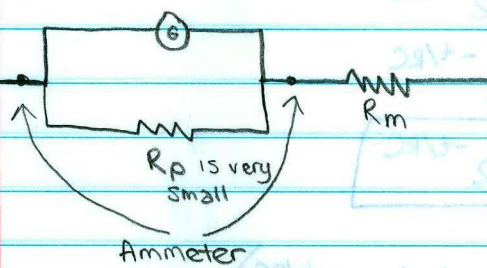- 1) in parallel
- 2) high resistance

Galvanometer - measures small currents  $R_G = 100 \Omega$



+120 V


0V

-120 V

(live)

(neutral) ground

(live)

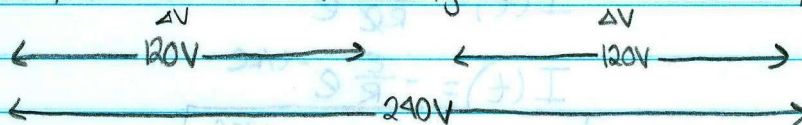

Problem 28-36 Circuit with Battery, 2 Resistors, Switch and Capacitor


14

AP Physics C – Video Lecture Notes

Chapter 27-28

Thank You, Emily Rencsok, for these notes.

28-36

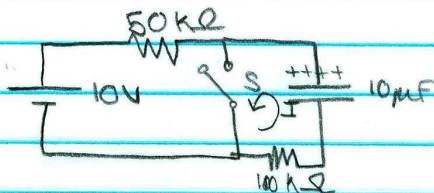

$t = \infty$  switch open

a)  $\tau = ?$  before switch is closed + after

b)  $I(t) = ?$  in switch after  $t = 0$  when switch is closed

$$\tau_{\text{before}} = RC \quad [R_{\text{before}} = R_{50} + R_{100}]$$

$$= (150 \times 10^3)(10 \times 10^{-6}) = 50 + 100 = 15 \text{ k}\Omega$$

$$\tau_b = 1.5 \text{ sec}$$

$$\tau_{\text{after}} = RC$$

$$= (100 \times 10^3)(10 \times 10^{-6})$$

$$\tau_a = 1.0 \text{ sec}$$

$$I_{\text{switch}} = I_e + I_c$$

$$\Delta V_c = \Delta V_{ci} = I_i R_{100}$$

$$\Delta V = IR$$

$$I_e = \frac{\Delta V_e}{R} = \frac{10}{50 \times 10^3}$$

$$I_e = 2 \times 10^{-4} \text{ A}$$

$$= 200 \mu\text{A}$$

$$I_c = I_0 e^{-t/RC} \text{ from } \tau_a$$


$$= (100 e^{-t/1}) \mu\text{A}$$

$$I_i = \Delta V_{ci} / R_{100}$$

$$I_i = \frac{10}{100 \times 10^3} = 100 \times 10^{-6} = 100 \mu\text{A}$$

$$I_{\text{switch}} = (200 + 100 e^{-t}) \mu\text{A}$$

$$= (0.200 + 0.100 e^{-t}) \text{ mA}$$

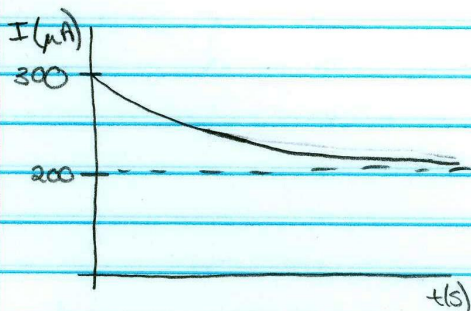



$$J = \frac{I}{A}$$

$$\Delta V_t + \text{emf, } \mathcal{E} \quad \Delta V_t = \mathcal{E} - Ir$$

(measured) (ideal)

## Kirchhoff's Rules

- 1)  $\Delta V_{\text{loop}} = 0$
- 2)  $\sum I_{\text{in}} = \sum I_{\text{out}}$

## Equations

matrix

ref

matrix answer

Ans w/ I dir

Check w/ extra loop

RC circuit
 $q(t) + I(t)$  charging + discharging

- 1) Derive
- 2) Limits
- 3) Graphs
- 4) Equations

## Ammeter + voltmeter

- where they go,  $\uparrow/\downarrow$  resistance