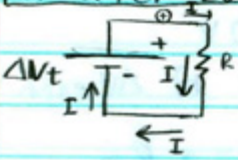


Thank You, Puja Patel, for these notes.


CHAPTER 20
 CHAPTER 20.1-20.3 - circuits & resistors



$\Delta V_t =$ terminal voltage
 $\text{emf} = \mathcal{E}$ ideal voltage
 resistance of wires = 0!!!

*current goes clockwise

Video Lecture #2 – Chapter 20.1 - Open, Closed and Short Circuits using an Incandescent Light Bulb




open circuit - no current flow
 closed circuit - current flow

short circuit = a circuit with very low resistance, bypassing the load.

Video Lecture #3 – Chapter 20.2 - Derivation of the Equivalent Resistance of Resistors in Series

2 resistors in series

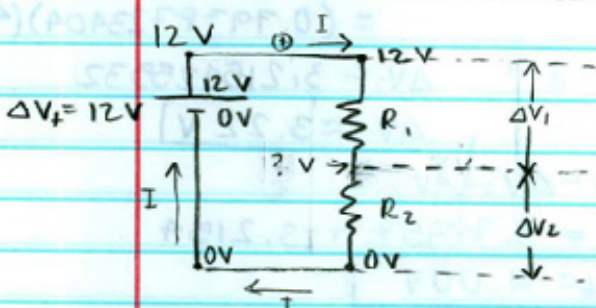

$\Delta V_t = \Delta V_1 + \Delta V_2$
 $I_t R_{eq} = \frac{I_1 R_1 + I_2 R_2}{I}$
 $R_{eq} = R_1 + R_2$

$I_t = I_1 = I_2$


$R_{series} = R_1 + R_2 + R_3 \dots$
 $I_t = I_1 = I_2$
 $\Delta V_t = \Delta V_1 + \Delta V_2 + \dots$

R_{eq} = equivalent resistance of the load

in series

$$p.739 \#4 \quad R_1 = 7.25 \, \Omega \quad \Delta V_t = 9.00 \, V$$
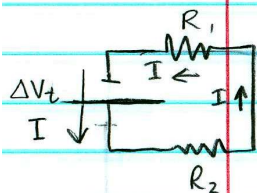
$$R_2 = 4.03 \, \Omega \quad a) R_{eq} = ? \quad b) \Delta V_{each} = ??$$



$$a) R_{eq} = R_1 + R_2$$

$$R_{eq} = (7.25 \, \Omega) + (4.03 \, \Omega)$$

$$R_{eq} = 11.28 \, \Omega$$

$$b) \Delta V_t = I_t R_{eq}$$

$$I_t = \frac{\Delta V_t}{R_{eq}}$$

$$I_t = \frac{(9.00)}{(11.28)}$$

$$I_t = 0.7978723404 \, A$$

$$= I_1 = I_2$$

$$\Delta V_1 = I_1 R_1$$

$$= (0.7978723404)(7.25)$$

$$\Delta V_1 = 5.784574468$$

$$\Delta V_1 \approx 5.78 \, V$$

$$\Delta V_2 = I_2 R_2$$

$$= (0.7978723404)(4.03)$$

$$\Delta V_2 = 3.215425532$$

$$\Delta V_2 \approx 3.22 \, V$$

$$\Delta V_t = \Delta V_1 + \Delta V_2$$

$$= 5.78457 + 3.2154$$

$$\Delta V_t = 9.00 \, V$$

2 resistors in parallel

$\Delta V_t = \Delta V_1 = \Delta V_2$
 $I_t = I_1 + I_2$
 $\Delta V = IR \Rightarrow I = \frac{\Delta V}{R}$

$$\frac{\Delta V_t}{R_{eq}} = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$

$\Delta V_t = \Delta V_1 = \Delta V_2$
 $I_t = I_1 + I_2$

P. 751 #1

$R_a = 5.0 \Omega$ $R_b = 7.0 \Omega$ $R_c = 4.0 \Omega$
 $R_d = R_e$ $R_f = 2.0 \Omega$ $\Delta V_t = 14.0 V$


$P_a = ? = I_a \Delta V_a = I_a^2 R_a = \frac{\Delta V_a^2}{R_a}$

$R_{ab} = R_a + R_b = 5 + 7 = 12 \Omega$

$R_{de} = \left(\frac{1}{R_d} + \frac{1}{R_e} \right)^{-1} = \left(\frac{1}{4} + \frac{1}{4} \right)^{-1} = 2 \Omega$

$R_{abc} = \left(\frac{1}{R_{ab}} + \frac{1}{R_c} \right)^{-1} = \left(\frac{1}{12} + \frac{1}{4} \right)^{-1}$


$R_{abc} = 3$

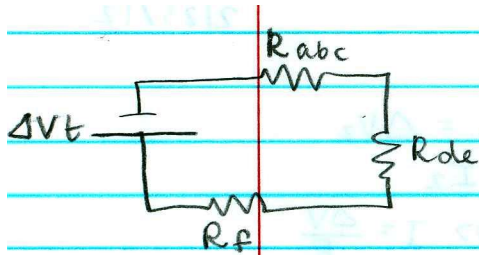

$$R_{eq} = R_{abc} + R_{de} + R_f$$

$$= (3) + (2) + (2)$$

$$R_{eq} = 7 \Omega$$

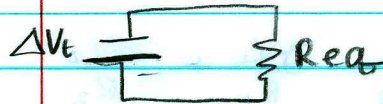

$$\Delta V = IR$$

$$\Delta V_t = I_t R_{eq}$$

$$I_t = \frac{\Delta V_t}{R_{eq}} = \frac{14}{7}$$

$$I_t = 2 \text{ A} = I_{ABC} = I_{DE} = I_f$$

$$\Delta V_{abc} = I_{abc} R_{abc}$$

$$\Delta V_{abc} = (2)(3) = 6 \text{ V} = \Delta V_{ab} = \Delta V_c$$

$$I_{ab} = \frac{\Delta V_{ab}}{R_{ab}} = \frac{6}{12} = 0.5 \text{ A} = I_A = I_B$$

$$P_a = I_a^2 R_a$$

$$= (0.5)^2 (5)$$

$$= 1.25$$

$$P_a \approx 1.2 \text{ watts}$$


* resistors in series = total will increase *

* resistors in parallel = total will decrease *

Video Lecture #7 – Chapter 20.3


A Complex Resistor Circuit: Part a) Drawing the Circuit Diagram and Finding Equivalent Resistance

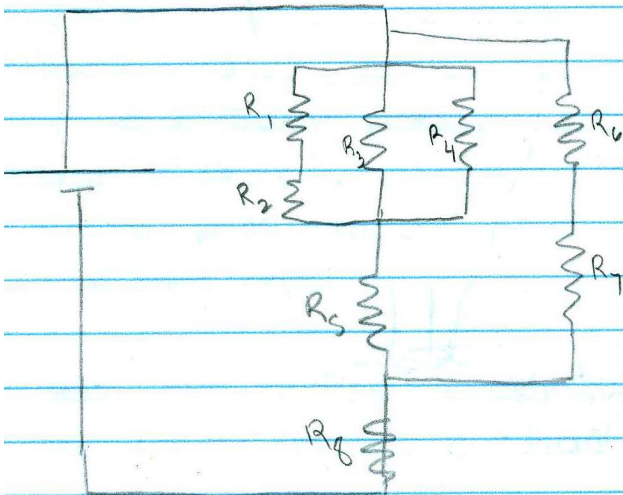Thank You, Sangini Tolia, for these notes.




$$R_{12} = R_1 + R_2 = 4 \Omega$$

$$R_{67} = R_6 + R_7 = 4 \Omega$$

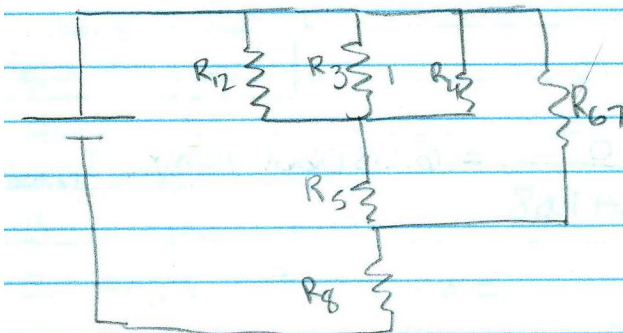

$$R_{1234} = \left(\frac{1}{R_{12}} + \frac{1}{R_3} + \frac{1}{R_4} \right)^{-1}$$

$$= 0.8 \Omega$$

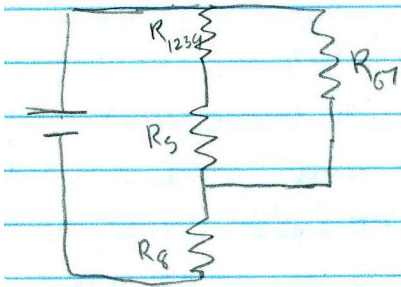



$$R_{12345} = R_{1234} + R_5$$

$$= 0.8 + 2$$

$$= 2.8 \Omega$$

$$R_{1234567} = \left(\frac{1}{R_{12345}} + \frac{1}{R_{67}} \right)^{-1}$$

$$= 1.6470587 \Omega$$

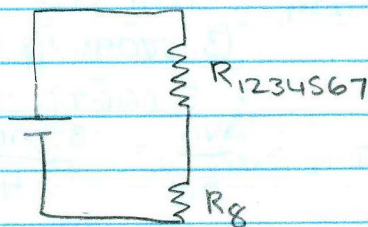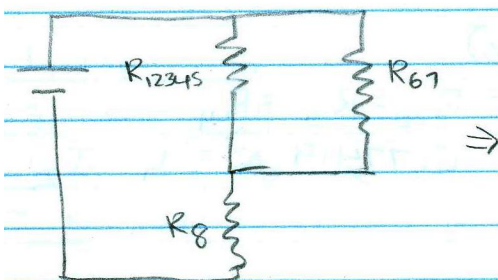

$$R_{eq} = R_{1234567} + R_8$$

$$= 1.647058 + 2$$

$$= 3.647058$$

$$= \boxed{3.65 \Omega}$$

Video Lecture #8 - Chapter 20.3
A Complex Resistor Circuit: Part b) Finding Power Dissipated in One Resistor

$$P = I \Delta V = I^2 R = \frac{\Delta V_1^2}{R_1}$$

$$\Delta V_t = 24.0 \text{ V}$$

$$R_{eq} = 3.647058$$

$$I_t = \frac{\Delta V_t}{R_{eq}} = \frac{24.0}{3.647058} = 6.580661 \text{ Amps} = I_{1234567} = I_8$$

$$\Delta V_{1234567} = I_{1234567} R_{1234567}$$

$$= 6.580661 (1.647058)$$

$$= 10.83871 \text{ V} = \Delta V_{12345} = \Delta V_{67}$$

$$\Delta V_{12345} = I_{12345} R_{12345}$$

$$10.83871 = I_{12345} (2.8)$$

$$3.870967 \text{ Amps } I_{12345} = I_{1234} = I_5$$

$$\Delta V_{1234} = I_{1234} R_{1234} = (3.870967)(0.8) = 3.09677 \Omega = \Delta V_{12} = \Delta V_3 = \Delta V_4$$

$$I_{12} = \frac{\Delta V_{12}}{R_{12}} = \frac{3.0967}{4} = 0.77419 \text{ A} = I_1 = I_2$$

$$P_1 = I_1^2 R_1$$

$$= (0.77419)(2)$$

$$= 1.12 \text{ W} \quad (\text{Power dissipated by } R_1)$$