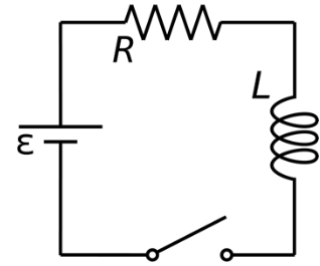


I'm not gonna lie, you really do need to have learned from these two previous lessons of mine in order to understand this:

- [LR Circuit Basics](#)
- [LR Circuit Equation Derivations](#)



LR Circuit:

- At $t_{\text{initial}} = 0$; $I_{\text{initial}} = 0$ & $\left(\frac{dI}{dt}\right)_{\text{initial}} = \frac{\epsilon}{L}$ [max value]
- At $t_{\text{final}} \approx \infty$; $I_f = \frac{\epsilon}{R}$ & $\left(\frac{dI}{dt}\right)_{\text{final}} = 0$ [max value]

$$I(t) = \frac{\epsilon}{R} \left(1 - e^{-\frac{Rt}{L}}\right) = I_{\text{max}} \left(1 - e^{-\frac{Rt}{L}}\right) \quad \& \quad \frac{dI}{dt}(t) = \frac{\epsilon}{L} e^{-\frac{Rt}{L}} = \left(\frac{dI}{dt}\right)_{\text{max}} e^{-\frac{Rt}{L}}$$

$$I(t) = \frac{\epsilon}{R} \left(1 - e^{-\frac{t}{\tau}}\right) \quad \& \quad \frac{dI}{dt}(t) = \frac{\epsilon}{L} e^{-\frac{t}{\tau}} \Rightarrow \tau = \frac{L}{R}$$

One time constant, τ , is the time it takes for a 63.2% change.

