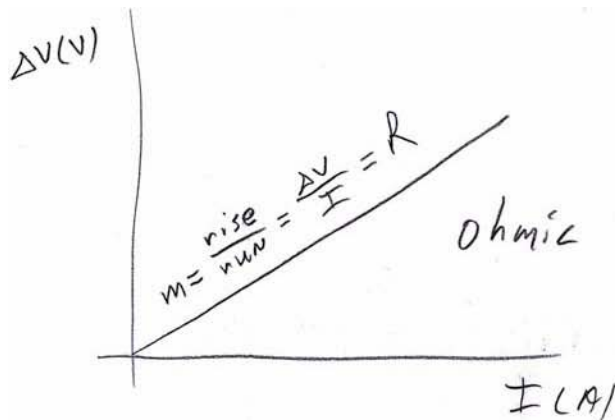




College Prep Physics II – Video Lecture Notes – Chapter 19
 Video Lecture #2
 Defining Resistance, Ohmic vs. Non-Ohmic, Electrical Power

Resistance, R , is the resistance to current flow. $R = \frac{\Delta V}{I} \Rightarrow \boxed{\Delta V = IR}$ (Ohm's Law)

$R = \frac{\Delta V}{I} \Rightarrow \frac{\text{Volts}}{\text{Amps}} = \Omega$ or Ohms (Capital Omega, an upside down horse shoe, it's unlucky.)



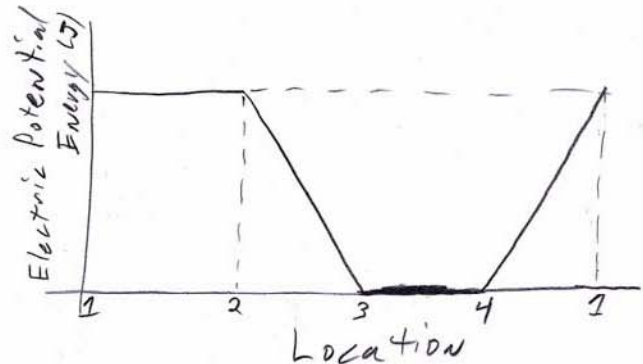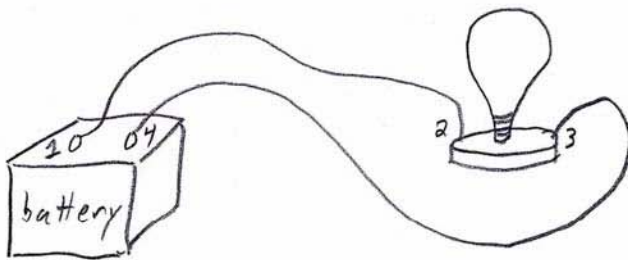Materials that follow Ohm's Law are called Ohmic. If they don't they are Non-Ohmic. We will consider all resistors to be Ohmic, unless otherwise stated.



Electric Power: The rate at which electrical potential energy is being converted to heat, light and sound.

From 1-2 and 3-4 the charges are moving along the wire and we consider wires to have zero resistance unless otherwise stated.

From 2-3 the electric potential energy of the electrons is converted to heat, light and sound.

From 4-1 the electrons are being given electric potential energy by the battery.

Derivation of Electric Power Equation:

$$P = \frac{W}{t} = \frac{\Delta PE_{electric}}{t} \Rightarrow \frac{J}{s} = \text{Watts} \quad \& \quad \Delta V = \frac{\Delta PE_{ele}}{q} \Rightarrow \Delta PE_{ele} = q\Delta V$$

$$\text{Therefore: } P = \frac{\Delta PE_{electric}}{t} = \frac{q\Delta V}{t} = \left(\frac{q}{t}\right)\Delta V = I\Delta V \quad \& \quad \Delta V = IR$$

$$\text{Gives: } P = I\Delta V = I(IR) = I^2R \quad \& \quad \Delta V = IR \Rightarrow I = \frac{\Delta V}{R}$$

$$\text{Gives: } P = I^2R = \left(\frac{\Delta V}{R}\right)^2 R = \frac{\Delta V^2 R}{R^2} = \frac{\Delta V^2}{R}$$

$$\text{Therefore: } \boxed{P = I\Delta V = I^2R = \frac{\Delta V^2}{R}}$$